



NAME:SAKETHVARMA SRINADHARAJU

REGISTER NUMBER:21BEC1416

COLLEGE:Vellore Institute of Technology-CHENNAI

## **Introduction**


Serial Peripheral Interface (SPI) is a master – slave type protocol that provides a simple and low cost interface between a microcontroller and its peripherals ICs such as sensors, ADC's, DAC's, shift register, SRAM and others. In SPI protocol, there can be only one master but many slave devices.

The SPI bus consists of 4 signals or pins. They are

- Master – Out / Slave – In (MOSI)
- Master – In / Slave – Out (MISO)
- Serial Clock (SCLK) and
- Slave Select (SS)

Data is exchanged simultaneously between devices in a serial manner (shifted out serially and shifted in serially). Serial clock line synchronizes shifting and sampling of information on two serial data lines. A slave select line allows individual selection of slave SPI devices.


## Architecture of SPI Master Core

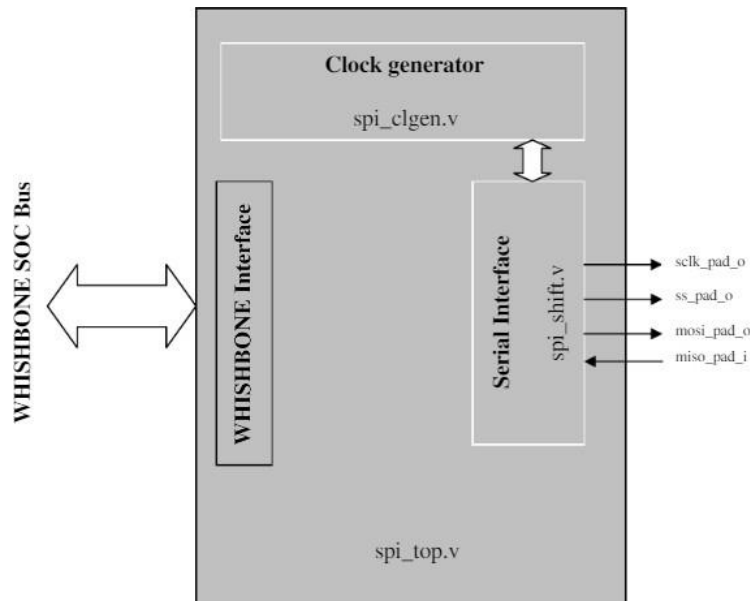

The SPI Master core consists of three parts shown in the following figure:

 
### Features of SPI Master Core:

- Full duplex synchronous serial data transfer
- Variable length of transfer word up to 128 bits
- MSB or LSB first data transfer
- Rx and Tx on both rising or falling edge of serial clock independently
- 8 slave select lines
- Fully static synchronous design with one clock domain
- Technology independent Verilog
- Fully synthesizable


 
### **SPI Master Core Interface:**

SPI Master Core module is a combination of clock generator and shift register blocks.



Module "spi.defines.v" is used to initialize all the variable values related to registers ( CTRL, SS, DIVIDER and SPI Registers).

Control and Status Register bus is as follows:

Bit #	31:14	13	12	11	10	9	8	7	6:0
Access	R	R/W	R/W	R/W	R/W	R/W	R/W	R	R/W
Name	Reserved	ASS	IE	LSB	Tx_NEG	Rx_NEG	GO_BSY	Reserved	CHAR_LEN

Slave Select Register bus is as follows:

Bit #	31:8	7:0
Access	R	R/W

Divider Register bus is as follows:


Bit #	31:16	15:0
Access	R	R/W
Name	Reserved	DIVIDER

TxX and RxX Register bus are as follows:

<b>Bit #</b>	31:0
<b>Access</b>	R/W
<b>Name</b>	Tx

<b>Bit #</b>	31:0
<b>Access</b>	R
<b>Name</b>	Rx

## Clock Generator Block:

 

Module Declaration: Defines the module spi\_clgen with input and output ports.

- Inputs:
  - ❖ wb\_clk\_in: Input clock signal.
  - ❖ wb\_rst: Reset signal.
  - ❖ go: Signal indicating the start of the transfer.
  - ❖ tip: Signal indicating whether a transfer is in progress.
  - ❖ last\_clk: Signal indicating the last clock edge of the transfer.
  - ❖ divider: Input value determining the clock divider for generating the SPI clock.
- Outputs:

- ❖ sclk\_out: indicating the pulse marking the positive edge of the SPI clock.  
Output SPI clock signal.
- ❖ cpol\_1: Output signal indicating the pulse marking the negative edge of the SPI clock.
- ❖ cpol\_0  
:  
Output  
signal

The clock generator block generates two clock signals: rx\_clk and tx\_clk. These clock signals are used to control the receive and transmit operations of the SPI shift register. The generation of these clocks is based on the input signals rx\_negedge, tx\_negedge, last, sclk, cpol\_0, and cpol\_1.

The value given to divider field is the frequency divider of the system clock wb\_clk\_i to generate the serial clock on the output sclk\_pad\_o. The desired frequency is obtained according to the following equation:

$$f_{sclk} = \frac{f_{wb\_clk}}{(DIVIDER+1)*2}$$

The rx\_clk signal is generated by combining the rx\_negedge input signal and the logical OR of last and sclk. It is used as the receive clock enable. The tx\_clk signal is generated by combining the tx\_negedge input signal and the logical AND of last and the selected clock polarity (cpol\_0 or cpol\_1). It is used as the transmit clock enable.

The clock generator block ensures that the clock signals are generated appropriately based on the specified clock polarities and the transfer status (last). This enables proper synchronization and timing control for the SPI shift register module during data transmission and reception.

### **Verilog Code for clock generator block:**

```
module spi_clgen (input wb_clk_in, wb_rst, go, tip, last_clk,
                 input [`SPI_DIVIDER_LEN-1:0]divider,
                 output reg sclk_out, cpol_0, cpol_1);
```

```

reg [`SPI_DIVIDER_LEN-1:0]cnt;
//Counter counts half period
always @(posedge wb_clk_in or posedge wb_rst)
begin
    if(wb_rst)
        cnt<={{`SPI_DIVIDER_LEN{1'b0}},1'b1};
    else if(tip)
        begin
            if(cnt==(divider+1))
                cnt<={{`SPI_DIVIDER_LEN{1'b0}},1'b1};
            else
                cnt<=cnt+1;
        end
    else if(cnt==0)
        cnt<={{`SPI_DIVIDER_LEN{1'b0}},1'b1};
end
//Generation of Serial clock
always @(posedge wb_clk_in or posedge wb_rst)
begin
    if(wb_rst)
        begin
            sclk_out<=1'b0;
        end
    else if(tip)
        begin
            if(cnt==(divider+1))
                begin
                    if(!last_clk|sclk_out)
                        sclk_out<=~sclk_out;
                end
        end
end
//Posedge and Negedge detection of sclk
always @(posedge wb_clk_in or posedge wb_rst)
begin

```


```

    if(wb_rst)
        begin
            cpol_0<=1'b0;
            cpol_1<=1'b0;
        end
    else
        begin
            cpol_0<=1'b0;
            cpol_1<=1'b0;
            if(tip)
                begin
                    if(~sclk_out)
                        begin
                            if(cnt==divider)
                                begin
                                    cpol_0<=1;
                                end
                            end
                        end
                    end
                end
            if(tip)
                begin
                    if(sclk_out)
                        begin
                            if(cnt==divider)
                                begin
                                    cpol_1<=1;
                                end
                            end
                        end
                    end
                end
            end
        end
    end
endmodule


```



## Clock generator Module Waveform

 

## Shift Register Block:

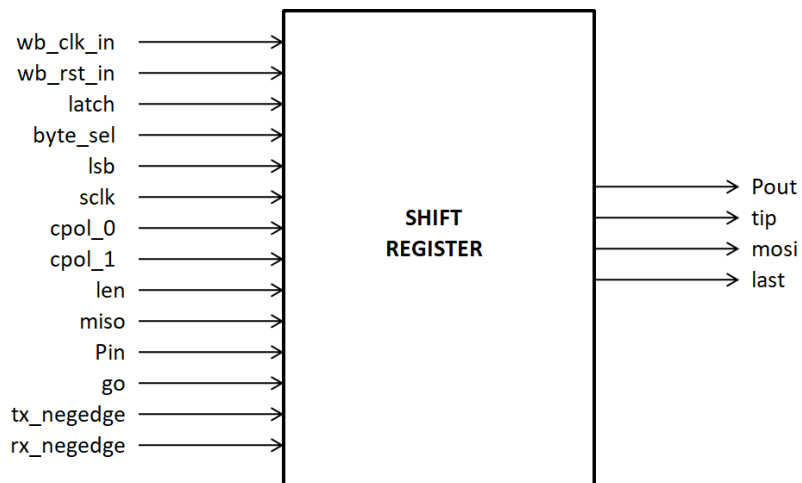

*Module Declaration: Defines the module spi\_shift\_register with input and output ports.*

- *Input:*
  - ❖ *rx\_negedge: Input signal, indicates the negative edge of the receive clock.*
  - ❖ *tx\_negedge: Input signal, indicates the negative edge of the transmit clock.*
  - ❖ *byte\_sel: 4-bit input signal used for byte selection.*
  - ❖ *latch: Input signal used for latch control.*
  - ❖ *len: 32-bit input signal representing the length of the character.*
  - ❖ *p\_in: 32-bit input signal for the incoming data.*
  - ❖ *wb\_clk\_in: Input clock signal (system clock).*
  - ❖ *wb\_rst: Input reset signal.*
  - ❖ *go: Input signal to initiate the transfer.*
  - ❖ *miso: Input signal for the master input slave output.*
  - ❖ *lsb: Input signal indicating the least significant bit.*
  - ❖ *cpol\_0: Input signal for the pulse marking the positive edge of the sclk\_out.*
  - ❖ *cpol\_1: Input signal for the pulse marking the negative edge of the sclk\_out.*
- *Output:*
  - ❖ *p\_out: Output signal representing the shifted data from the shift register. It is SPI\_MAX\_CHAR bits wide.*
  - ❖ *last: Output signal indicating whether the last character is being transmitted or received.*
  - ❖ *mosi: Output signal representing the serial output data from the shift register.*
  - ❖ *tip: Output signal indicating if a transfer is in progress or not.*
  - ❖ *rx\_clk: Output signal representing the receive clock enable.*
  - ❖ *tx\_clk: Output signal representing the transmit clock enable.*
- *Internal Registers:*
  - ❖ *char\_count: Register used for counting the number of bits in a character.*
  - ❖ *master\_data: Register representing the shift register holding the data.*
  - ❖ *tx\_bit\_pos: Register indicating the next bit position for transmission.*
  - ❖ *rx\_bit\_pos: Register indicating the next bit position for reception.*

*The shift register module takes various inputs such as clock signals, data selection, data input, and control signals. The module includes internal registers for storing data, bit positions for data shifting, and a counter for character bit tracking.*

*It calculates the transfer in progress and the last character indicator. It also calculates the serial output based on the clock signals and the current bit position.*

*The module handles the calculation of the bit positions for both transmission and reception based on the configuration. The output is the shifted data from the shift register. The module also supports data latching.*

### **Verilog Code for Shift Registers:**

```
module
spi_shift_reg(tx_negedge,rx_negedge,byte_sel,latch,len,p_in,wb_clk_in,wb_rst,go,miso,lsb,sclk
,cpol_0,cpol_1,p_out,last,mosi,tip);

input tx_negedge,rx_negedge,wb_clk_in,wb_rst,go,miso,lsb,sclk,cpol_0,cpol_1;

input [3:0] byte_sel,latch;

input [`SPI_CHAR_LEN_BITS-1:0] len;

input [31:0] p_in;

output [`SPI_MAX_CHAR-1:0] p_out;

output reg tip,mosi;

output last;

reg [`SPI_CHAR_LEN_BITS:0] char_count;

reg [`SPI_MAX_CHAR-1:0] master_data;

reg [`SPI_CHAR_LEN_BITS:0] tx_bit_pos;

reg [`SPI_CHAR_LEN_BITS:0] rx_bit_pos;

wire rx_clk;

wire tx_clk;
```

```

//Character bit counter.....

always @(posedge wb_clk_in or posedge wb_rst)

begin

    if(wb_rst)

        begin

            char_count <= 0;

        end

    else

        begin

            if(tip)

                begin

                    if(cpol_0)

                        begin

                            char_count<=char_count-1;

                        end

                    end

                end

            else

                char_count <= {1'b0,len};

            end

        end

    end

//Calculate transfer in progress

always @(posedge wb_clk_in or posedge wb_rst)

begin

```

```

if(wb_rst)

begin

    tip <= 0;

end

else

begin

    if(go && ~tip)

begin

    tip <=1;

end

    else if(last && tip && cpol_0)

begin

    tip <=0;

end

end

end

end

//calculate last

assign last= ~(|char_count);

//calculate the serial out.....

always@ (posedge wb_clk_in or posedge wb_rst)

begin

    if(wb_rst)

begin

```

```

mosi <=0;

    end

else

    begin

        if(tx_clk)

            begin

                mosi <= master_data[tx_bit_pos[`SPI_CHAR_LEN_BITS-1:0]];

            end

        end

    end

end

//calculate tx_clk,rx_clk.....

assign tx_clk = ((tx_negedge)?cpol_1: cpol_0) && !last;

assign rx_clk = ((rx_negedge)?cpol_1: cpol_0) &&(!last || sclk);

//calculate TX_BIT Position.....

always@ (lsb,len,char_count)

begin

    if(lsb)

        begin

            tx_bit_pos = ({~{len},len}-char_count);

        end

    else

        begin

            tx_bit_pos = char_count-1

        end

    end

end

```

end

end

//Calculate RX\_BIT Position ..... based on rx\_negedge as miso depends on rxclk .....

always @(lsb, len, rx\_negedge, char\_count)

begin

if(lsb)

begin

if(rx\_negedge)

rx\_bit\_pos = {~{|len|},len}-(char\_count+1);

else

rx\_bit\_pos = {~{|len|},len}-char\_count;

end

else

begin

if(rx\_negedge)

begin

rx\_bit\_pos=char\_count;

end

else

begin

rx\_bit\_pos = char\_count-1;

end

```

        end

    end

    //calculate p_out.....

    assign p_out = master_data;

    //latching of data.....

    always @(posedge wb_clk_in or posedge wb_rst)
    begin
        if(wb_rst)
            master_data <= `{SPI_MAX_CHAR{1'b0}};

        //Receiving bits from the parallel line.....

        `ifdef SPI_MAX_CHAR_128

        else if(latch[0] && !tip) //TX0 is selected..
        begin
            if(byte_sel[0])
            begin
                master_data[7:0] <= p_in [7:0];
            end

            if(byte_sel[1])

```



```

begin

    master_data[15:8] <= p_in [15:8];

end

if(byte_sel[2])

    begin

        master_data[23:16] <= p_in [23:16];

    end

if(byte_sel[3])

    begin

        master_data[31:24] <= p_in [31:24];

    end

end

end

else if(latch[1] && !tip) //TX1 is selected

begin

    if(byte_sel[0])

        begin

            master_data[39:32] <= p_in [7:0];

        end

    if(byte_sel[1])

        begin

            master_data[47:40] <= p_in [15:8];

        end

    end

end

```

```

if(byte_sel[2])
    begin
        master_data[55:48] <= p_in [23:16];
    end
if(byte_sel[3])
    begin
        master_data[63:56] <= p_in [31:24];
    end
end

```

else if(latch[2] && !tip) //TX2 is selected..

```

begin
    if(byte_sel[0])
        begin
            master_data[71:64] <= p_in [7:0];
        end
    if(byte_sel[1])
        begin
            master_data[79:72] <= p_in [15:8];
        end
    if(byte_sel[2])
        begin
            master_data[87:80] <= p_in [23:16];

```

```

        end

    if(byte_sel[3])

        begin

            master_data[95:88] <= p_in [31:24];

        end

    end

else if(latch[3] && !tip) //TX3 is selected..

    begin

        if(byte_sel[0])

            begin

                master_data[103:96] <= p_in[7:0];

            end

        if(byte_sel[1])

            begin

                master_data[111:104] <= p_in[15:8];

            end

        if(byte_sel[2])

            begin

                master_data[119:112] <= p_in[23:16];

            end

        if(byte_sel[3])

            begin

```

```

        master_data[127:120] <= p_in[31:24];

    end

end

`else

`ifdef SPI_MAX_CHAR_64

else if(latch[0] && !tip) //TX0 is selected..

begin

    if(byte_sel[0])

        begin

            master_data[7:0] <= p_in[7:0];

        end

        if(byte_sel[1])

            begin

                master_data[15:8] <= p_in[15:8];

            end

            if(byte_sel[2])

                begin

                    master_data[23:16] <= p_in[23:16];

                end

                if(byte_sel[3])

```

```

begin
    master_data[31:24] <= p_in[31:24];
end
end

```

else if(latch[1] && !tip)//TX1 is selected..

```

begin
    if(byte_sel[0])
        begin
            master_data[39:32] <= p_in[7:0];
        end
    if(byte_sel[1])
        begin
            master_data[47:40] <= p_in[15:8];
        end
    if(byte_sel[2])
        begin
            master_data[55:48] <= p_in[23:16];
        end
    if(byte_sel[3])
        begin
            master_data[63:56] <= p_in[31:24];
        end
    end

```

end

`else

else if(latch[0] && !tip)//TX0 is selected..

begin

`ifdef SPI\_MAX\_CHAR\_8

if(byte\_sel[0])

begin

master\_data[7:0] <= p\_in[7:0];

end

`endif

`ifdef SPI\_MAX\_CHAR\_16

if(byte\_sel[0])

begin

master\_data[7:0] <= p\_in[7:0];

end

if(byte\_sel[1])

begin

master\_data[15:8] <= p\_in[7:0];

end

`endif

```

`ifdef SPI_MAX_CHAR_24

if(byte_sel[0])

begin

master_data[7:0] <= p_in[7:0];

end


if(byte_sel[1])

begin

master_data[15:8] <= p_in[7:0];

end


if(byte_sel[2])

begin

master_data[23:16] <= p_in[23:16];

end


`endif


`ifdef SPI_MAX_CHAR_32

if(byte_sel[0])

begin

```

```

        master_data[7:0] <= p_in[7:0];

    end

    if(byte_sel[1])

        begin

            master_data[15:8] <= p_in[7:0]; //I think here it should be 15:8

        end

    if(byte_sel[2])

        begin

            master_data[23:16] <= p_in[23:16];

        end

    if(byte_sel[3])

        begin

            master_data[31:24] <= p_in[31:24];

        end

    `endif

end

`endif

`endif

```

//Receiving bit from serial line.....

```

else


```




endmodule

## Shift Register Module Waveforms

MISO

 

MOSI

 

## SPI Top Block

It interfaces with a Wishbone bus and provides communication with a master device using the SPI protocol.

- Inputs:
  - ❖ `wb_clk_in`: Clock input for the Wishbone bus.
  - ❖ `wb_rst_in`: Reset input for the Wishbone bus.
  - ❖ `wb_adr_in`: Address input for the Wishbone bus.
  - ❖ `wb_dat_in`: Data input for the Wishbone bus.
  - ❖ `wb_sel_in`: Select input for the Wishbone bus.
  - ❖ `wb_we_in`: Write enable input for the Wishbone bus.
  - ❖ `wb_stb_in`: Strobe input for the Wishbone bus.
  - ❖ `wb_cyc_in`: Cycle input for the Wishbone bus.
  - ❖ `miso`: Master Input Slave Output (MISO) signal
- Outputs:
  - ❖ `wb_dat_o`: Data output for the Wishbone bus.
  - ❖ `wb_ack_out`: Acknowledge output for the Wishbone bus.
  - ❖ `wb_int_o`: Interrupt output for the Wishbone bus.
  - ❖ `sclk_out`: Clock output for the SPI interface.
  - ❖ `mosi`: Master Output Slave Input (MOSI) signal.
  - ❖ `ss_pad_o`: Slave select output for the SPI interface.

The code instantiates two sub-modules: `"spi_clgen"` and `"spi_shift_reg"`.

- `"spi_clgen"` generates the SPI clock signal based on the input clock and control signals.
- `"spi_shift_reg"` handles the data shifting and synchronization for SPI communication.

It decodes addresses to read from specific registers and provides output data and acknowledgment signals. It also supports interrupt generation and slave device selection. Overall, it serves as a complete SPI controller for data transfer between a master and multiple slave devices.

## Wishbone Master Module Interface

SPI Master acts as a slave to Wishbone Interface. Wishbone master communicates with the host. Bus signals of Wishbone master are as follows:

Port	Width	Direction	Description
wb_clk_i	1	Input	Master clock
wb_rst_i	1	Input	Synchronous reset, active high
wb_adr_i	5	Input	Lower address bits
wb_dat_i	32	Input	Data towards the core
wb_dat_o	32	Output	Data from the core
wb_sel_i	4	Input	Byte select signals
wb_we_i	1	Input	Write enable input
wb_stb_i	1	Input	Strobe signal/Core select input
wb_cyc_i	1	Input	Valid bus cycle input
wb_ack_o	1	Output	Bus cycle acknowledge output
wb_err_o	1	Output	Bus cycle error output
wb_int_o	1	Output	Interrupt signal output

Table 1: Wishbone interface signals

All output WISHBONE signals are registered and driven on the rising edge of wb\_clk\_i. All input WISHBONE signals are latched on the rising edge of wb\_clk\_i.

Module Declaration: Defines the module wishbone\_master with input and output ports.

- Inputs:
  - ❖ clk\_in: The clock input for the module.
  - ❖ rst\_in: The reset input for the module.
  - ❖ ack\_in: The acknowledgment input from the slave device.
  - ❖ err\_in: The error input from the slave device.
  - ❖ dat\_in: The data input for write operations.

- Outputs:
  - ❖ `adr_o`: The address output for the Wishbone master.
  - ❖ `cyc_o`: The cycle output for initiating a Wishbone transaction.
  - ❖ `stb_o`: The strobe output for indicating the start of a Wishbone transaction.
  - ❖ `we_o`: The write enable output for write operations.
  - ❖ `dat_o`: The data output for read operations.
  - ❖ `sel_o`: The select output for selecting the active byte lanes.

The module contains a task called "initialize" for initializing the internal signals of the module. It also contains a task called `single_write` for performing a single write operation. It sets the internal signals `adr_temp`, `sel_temp`, `we_temp`, `dat_temp`, `cyc_temp`, and `stb_temp` based on the provided inputs. It waits for the acknowledgment signal (`ack_in`) to go low before resetting the internal signals.


The module uses sequential blocks (`always@(posedge clk_in)`) to assign values to the output signals based on the internal signals. The `rst_in` signal is used to handle reset conditions for `cyc_o` and `stb_o`.

Overall, the `wishbone_master` module provides control and data signals for interacting with a Wishbone slave device, allowing for read and write operations.
 
## Slave Module Interface

The master can choose which slave it wants to talk to by setting the slave's SS line to a low voltage level. In the idle, non-transmitting state, the slave select line is kept at a high voltage level. Multiple SS pins may be available on the master, which allows for multiple slaves to be wired in parallel. If only one SS pin is present, multiple slaves can be wired to the master by daisy-chaining.

SPI Slave module here just behaves as a "slave" to test for the code results. It is not an actual slave.



Bus Signals for SPI slave module are as follows:

Port	Width	Direction	Description
/ss_pad_o	8	Output	Slave select output signals
sclk_pad_o	1	Output	Serial clock output
mosi_pad_o	1	Output	Master out slave in data signal output
miso_pad_i	1	Input	Master in slave out data signal input

**Table 2: SPI external connections**

Module Declaration: Defines the module spi\_slave with input and output ports.

- Inputs:
  - ❖ sclk: The serial clock input for synchronization.
  - ❖ mosi: The input signal representing the data received from the SPI master.
  - ❖ ss\_pad\_o: A multi-bit output signal representing the chip select lines for the SPI slave.
- Output:
  - ❖ miso: The output signal representing the data to be transmitted from the SPI slave.
- Internal signals:
  - ❖ rx\_slave: A register indicating whether the SPI slave is in receive mode.
  - ❖ tx\_slave: A register indicating whether the SPI slave is in transmit mode.
  - ❖ temp1: A 128-bit register used for temporary storage of received data.
  - ❖ temp2: A 128-bit register used for temporary storage of received data.

On the posedge of sclk, if the chip select lines are not all high (ss\_pad\_o != 8'b1111111) and the slave is in receive mode (rx\_slave is high) and not in transmit mode (tx\_slave is low), the received data mosi is concatenated with the existing data in temp1.

On the negedge of sclk, if the slave is in receive mode (rx\_slave is high) and not in transmit mode (tx\_slave is low), the value in temp1 is assigned to miso1.


On the posedge of sclk, if the slave is in receive mode (rx\_slave is high) and not in transmit mode (tx\_slave is low), the value in temp2 is assigned to miso2.


The miso signal is assigned as the logical OR of miso1 and miso2, which represents the data to be transmitted from the SPI slave.

Overall, the spi\_slave module receives data from the SPI master on the mosi line, processes and stores it in temp1 and temp2, and provides the output miso for transmitting data back to the SPI master. The chip select lines (ss\_pad\_o) are used to control the slave operation.


## Test Case Module Waveforms

### A. RX negedge = 1 and TX negedge = 0

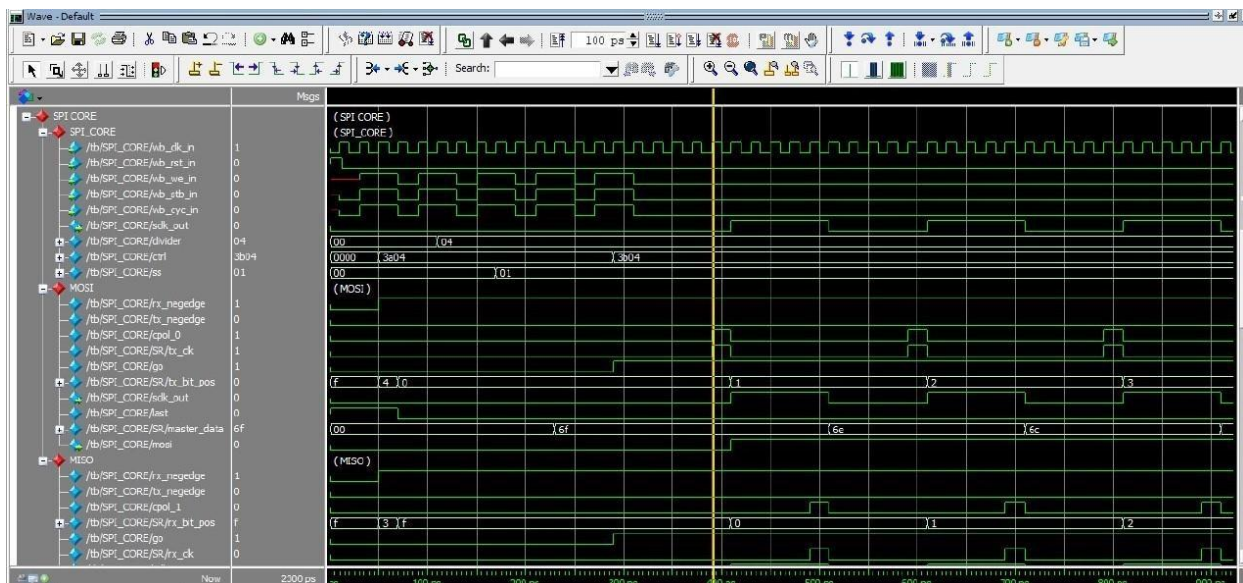

 



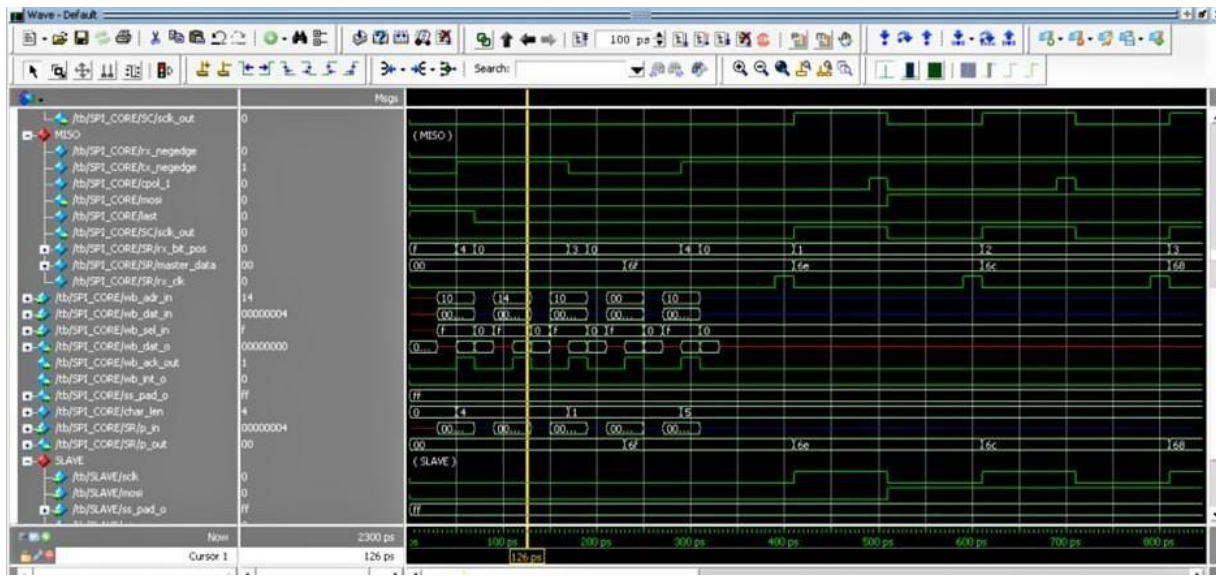

### Verilog code for spi Wishbone Master:

```
module wishbone_master(input clk_in, rst_in, ack_in, err_in, input [31:0]dat_in,
                        output reg [4:0]adr_o, output reg cyc_o, stb_o, we_o,
                        output reg [31:0]dat_o, output reg [3:0]sel_o);
```

```
//Internal Signals.....
```

```
integer adr_temp, sel_temp, dat_temp;
```

```
reg we_temp, cyc_temp, stb_temp;
```

```
//Initialise task.....
```

```
task initialize;
```

begin

```
{adr_temp, cyc_temp, stb_temp, we_temp, dat_temp, sel_temp}=0;
```

end

endtask

```
//Wishbone Bus Cycles Single Read/Write
```

```
task single_write;
```

```
input [4:0]adr;
```

```
input [31:0]dat;
```

```
input [3:0]sel;
```

begin

```
@(negedge clk_in);
```

```
adr_temp = adr;
```

```
sel_temp = sel;
```

```
we temp = 1;
```

```
dat_temp = dat;
```

```
cyc_temp = 1;
```

```
stb_temp = 1;
```

```
@(negedge clk_in);
```



```

        wait(~ack_in)
        @(negedge clk_in);
        adr_temp = 5'dz;
        sel_temp = 4'd0;
        we_temp = 1'b0;
        dat_temp = 32'dz;
        cyc_temp = 1'b0;
        stb_temp = 1'b0;
    end
endtask

always @(posedge clk_in)
begin
    adr_o <= adr_temp;
end

always @(posedge clk_in)
begin
    we_o <= we_temp;
end

always @(posedge clk_in)
begin
    dat_o <= dat_temp;
end

always @(posedge clk_in)
begin
    sel_o <= sel_temp;
end

always @(posedge clk_in)
begin
    if(rst_in)
        cyc_o <= 0;
    else
        cyc_o <= cyc_temp;
    end
always @(posedge clk_in)
begin
    if(rst_in)
        stb_o <= 0;
    else
        stb_o <= stb_temp;
    end
endmodule

```

### Verilog Code for Slave:

```
module spi_slave(sclk,mosi,ss_pad_o,miso);
input sclk,mosi;
input [`SPI_SS_NB-1:0]ss_pad_o;
output miso;
reg rx_slave =1'b0;
reg tx_slave=1'b0;

reg[127:0]temp1=0;
reg[127:0]temp2=0;

reg miso1=1'b0;
reg miso2=1'b1;

always@(posedge sclk)
begin
if((ss_pad_o != 8'b11111111) && ~rx_slave && tx_slave)
begin
temp1<={temp1[126:0],mosi};
end
end

always@(negedge sclk)
begin
if((ss_pad_o != 8'b11111111) && rx_slave && ~tx_slave)
begin
temp2<={temp2[126:0],mosi};
end
end

always@(negedge sclk)
begin
if(rx_slave && ~tx_slave)
begin
miso1<=temp1[127];
end
end

always@(posedge sclk)
begin
if(~rx_slave && tx_slave)
begin
miso2<=temp2[127];
end
end
end
```

```
assign miso= miso1 || miso2;
endmodule
```

### **SPI TEST BENCH:**

```
module tb;
reg wb_clk_in, wb_rst_in;
wire wb_we_in,wb_stb_in, wb_cyc_in,miso;

wire [4:0] wb_adr_in;
wire [31:0] wb_dat_in;
wire [3:0] wb_sel_in;

wire [31:0] wb_dat_o;

wire wb_ack_out, wb_int_o, sclk_out, mosi;

wire [`SPI_SS_NB-1:0] ss_pad_o;

parameter T=20;

    wishbone_master MASTER(wb_clk_in,wb_rst_in, wb_ack_out, wb_err_in, wb_dat_o,
wb_adr_in, wb_cyc_in, wb_stb_in, wb_we_in, wb_dat_in, wb_sel_in);

spi_top SPI_CORE(wb_clk_in,wb_rst_in, wb_adr_in, wb_dat_o, wb_sel_in,
wb_we_in,wb_stb_in,wb_cyc_in,wb_ack_out,wb_int_o,
wb_dat_in,ss_pad_o,sclk_out,mosi,miso);

spi_slave SLAVE(sclk_out,mosi,ss_pad_o,miso);

initial
begin
wb_clk_in =1'b0;
forever
#(T/2) wb_clk_in = ~wb_clk_in;
end

task rst;
begin
wb_rst_in =1'b1;
#13;
wb_rst_in=1'b0;
end
endtask

//tx_neg=1, rx_neg=0,lsb=1,char_len=4
36
```

```

/*initial
begin
rst;
//initialize the WISHBONE output signals
MASTER.initialize;
//configure control register with go_busy being low
MASTER.single_write(5'h10,32'h0000_3C04,4'b1111);
//configure divider with go_busy being low
MASTER.single_write(5'h14,32'h0000_0004,4'b1111);
//configure slave register with go_busy being low
MASTER.single_write(5'h18,32'h0000_0001,4'b1111);
//configure tx register with go_busy being low and processor is sending 4 bits
MASTER.single_write(5'h00,32'h0000_236f,4'b1111);
//configure control register with go_busy being high
MASTER.single_write(5'h10,32'h0000_3d04,4'b1111);
repeat(100)
@(negedge wb_clk_in);
$finish;
#10000
$finish;
end*/

```

```

//tx_neg=1, rx_neg=0, LSB =0, char_len=4
/*initial
begin
rst;
//initialize the WISHBONE output signals
MASTER.initialize;
//configure control register with go_busy being low
MASTER.single_write(5'h10, 32'h0000_3404, 4'b1111);
//configure slave register with go_busy being low
MASTER.single_write(5'h14, 32'h0000_0004, 4'b1111);
//configure slave register with go_busy being low
MASTER.single_write(5'h18, 32'h0000_0001, 4'b1111);
//configure the tx register with go_busy being low and processor is sending 4 bits
MASTER.single_write(5'h00, 32'h0000_26ff, 4'b1111);
//configure control register with go_busy high
MASTER.single_write(5'h10, 32'h0000_3504, 4'b1111);
repeat(100)
@(negedge wb_clk_in);
$finish;
#10000
$finish;
end*/

```

```

//tx_neg=0, rx_neg=1, LSB=1,char_len=4

```

```

/*initial
begin
rst;
//initialize the WISHBONE output signals
MASTER.initialize;
//configure control register with go_busy low
MASTER.single_write(5'h10,32'h0000_3A04,4'b1111);
//configure divider with go_busy low
MASTER.single_write(5'h14,32'h0000_0004,4'b1111);
//configure slave register with go_busy being low
MASTER.single_write(5'h18,32'h0000_0001,4'b1111);
//configure tx register with go_busy being low and processor is sending 4 bits
MASTER.single_write(5'h00,32'h0000_236f,4'b1111);
//configure control register with go_busy being high
MASTER.single_write(5'h10,32'h0000_3B04,4'b1111);
repeat(100)
@(negedge wb_clk_in);
//$finish;
#10000
//$finish;*/

```

```

//tx_neg =0, rx_neg = 1,LSB=0, char_len=4
initial
begin
rst;
//initialize the WISHBONE output signals
MASTER.initialize;
//configure control register with go_busy low
MASTER.single_write(5'h10,32'h0000_3204,4'b1111);
//configure divider with go_busy low
MASTER.single_write(5'h14,32'h0000_0004,4'b1111);
//configure slave register with go_busy being low
MASTER.single_write(5'h18,32'h0000_0001,4'b1111);
//configure tx register with go_busy being low and processor is sending 4 bits
MASTER.single_write(5'h00,32'h0000_236f,4'b1111);
//configure control register with go_busy being high
MASTER.single_write(5'h10,32'h0000_3304,4'b1111);
repeat(100)
@(negedge wb_clk_in);
$finish;
#10000
$finish;
end

```

```
initial
begin
  /*//tx_neg=1, rx_neg = 0
  SLAVE.rx_slave=0;
  SLAVE.tx_slave=1;*/

  //tx_neg=0, rx_neg=1
  SLAVE.rx_slave=1;
  SLAVE.tx_slave=0;
end
endmodule
```